

T.P. 5

P.7

ϵ_2 capacitor ambos espuñadores


$$C_1 = 5 \mu F$$

$$\Delta V_1 = 200 V$$

$$C_2 = 2 \mu F$$


$$\Delta V_2 = 130 V$$

$$F = \frac{C}{V}$$

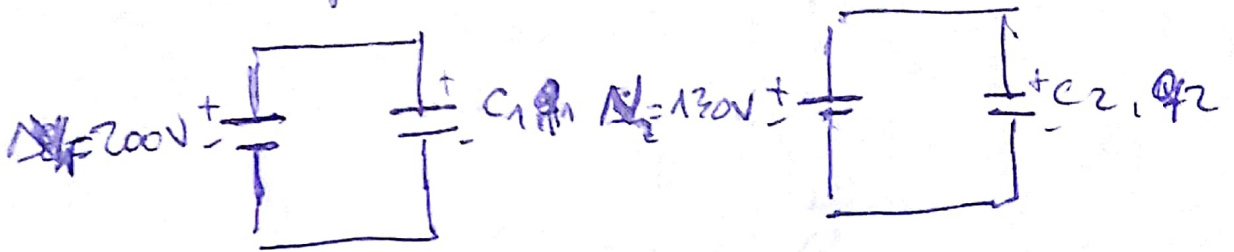

$$q_1 = C_1 \Delta V_1 = 5 \cdot 10^{-6} F \cdot 200 V = 1 mC$$
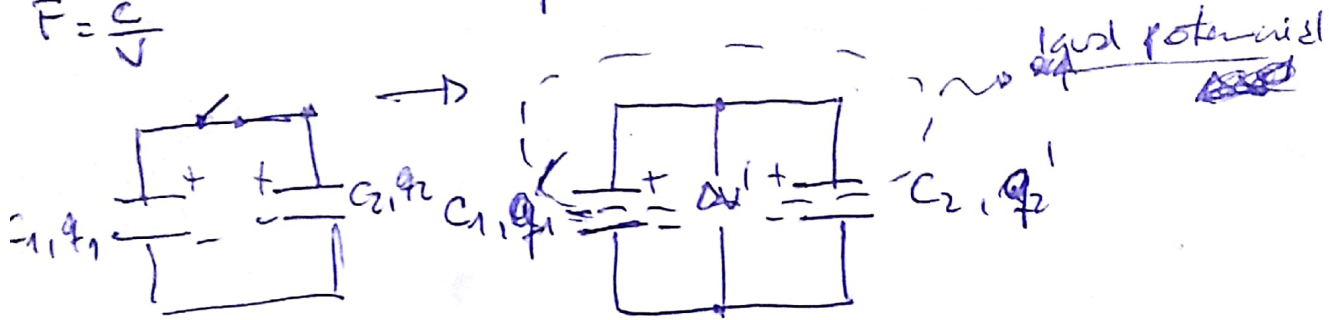
$$q_2 = C_2 \Delta V_2 = 2 \cdot 10^{-6} F \cdot 130 V = 0,26 mC$$



$$q_{total} = q_1 + q_2 = q_1' + q_2' = 1,26 mC$$



$$q_{total} = q_1' + q_2' = C_1 \Delta V' + C_2 \Delta V' = (C_1 + C_2) \Delta V'$$

$$q_{total} = (C_1 + C_2) \Delta V' = C_{eq} \cdot \Delta V'$$

$$\Delta V' = \frac{q_{total}}{C_1 + C_2} = \frac{1,26 mC}{5 \cdot 10^{-6} F + 2 \cdot 10^{-6} F} = 180 V$$

$$q_1' = C_1 \Delta V' = 5 \cdot 10^{-6} F \cdot 180 V = 0,9 mC$$
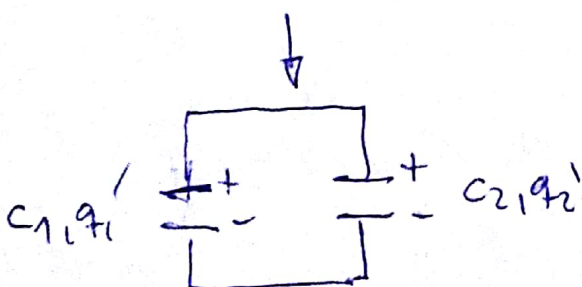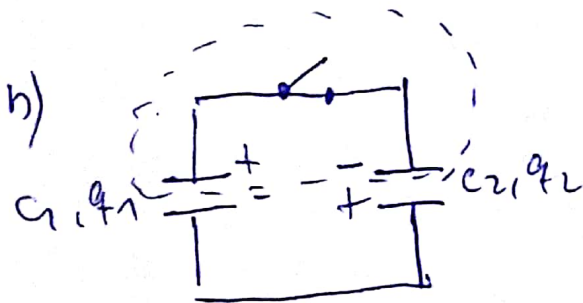
$$q_2' = C_2 \Delta V' = 2 \cdot 10^{-6} F \cdot 180 V = 0,36 mC$$



$$q_{total} = q_1 - q_2 = q_1' + q_2' = 0,74 mC$$

$$q_{total} = q_1' + q_2' = C_1 \Delta V' + C_2 \Delta V'$$

$$q_{total} = (C_1 + C_2) \Delta V'$$

$$\Delta V' = \frac{q_{total}}{C_1 + C_2} = \frac{0,74 mC}{7 \cdot 10^{-6} F} = 105,7 V$$

$$q_1' = C_1 \Delta V' = 5 \cdot 10^{-6} F \cdot 105,7 V = 0,528 mC$$

$$q_2' = C_2 \Delta V' = 2 \cdot 10^{-6} F \cdot 105,7 V = 0,211 mC$$